

Chapter # 4: Programmable and Steering Logic

4-1

Chapter Overview


- *PALs and PLAs*
- *Non-Gate Logic*
 - Switch Logic
 - Multiplexers/Selectors and Decoders
 - Tri-State Gates/Open Collector Gates
 - ROM
- *Combinational Logic Design Problems*
 - Seven Segment Display Decoder
 - Process Line Controller
 - Logical Function Unit
 - Barrel Shifter

4-2

PALs and PLAs

Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
"Personalized" by making or breaking connections among the gates

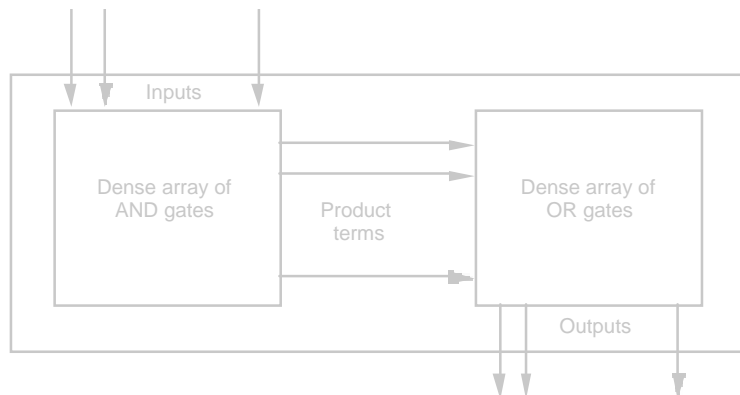Programmable Array Block Diagram for Sum of Products Form



4-3

PALs and PLAs

Key to Success: Shared Product Terms

Equations

Example:

$$\begin{aligned} F_0 &= A + B' C' \\ F_1 &= A C' + A B \\ F_2 &= B' C' + A B \\ F_3 &= B' C + A \end{aligned}$$

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
AB	1	1	-	0	1	1	0
$\overline{B}C$	-	0	1	0	0	0	1
$\overline{A}C$	1	-	0	0	1	0	0
$\overline{B}C$	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

Reuse of terms

Input Side:


1 = asserted in term
0 = negated in term
- = does not participate

Output Side:


1 = term connected to output
0 = no connection to output

4-4

PALs and PLAs

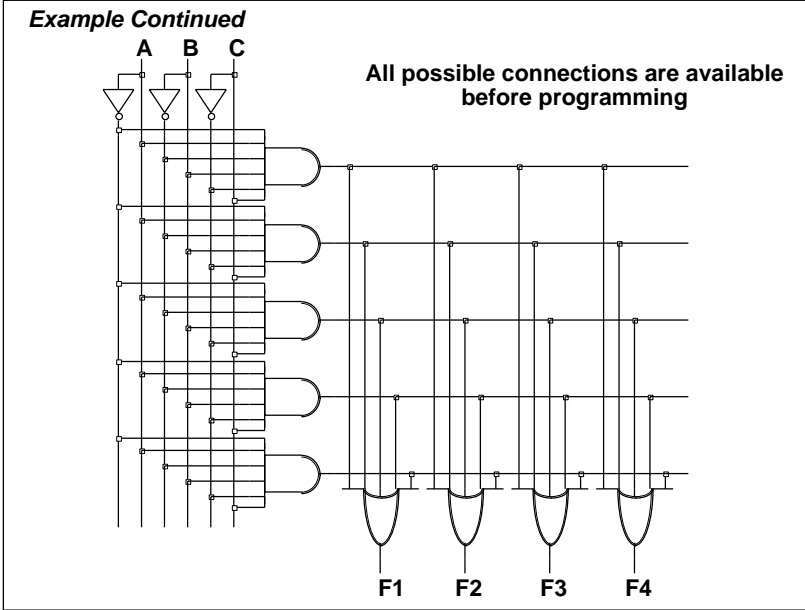


PALs and PLAs

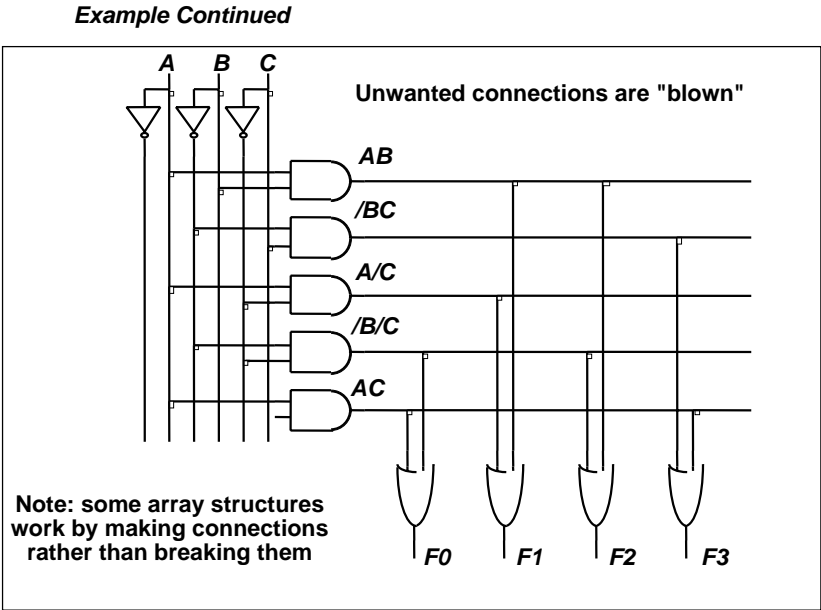


PALs and PLAs

 Alternative representation for high fan-in structures



 Short-hand notation
so we don't have to
draw all the wires!



PALs and PLAs

Design Example

Multiple functions of A, B, C

$F1 = A B C$


$F2 = A + B + C$

$F3 = \overline{A} B C$

$F4 = A + B + C$

$F5 = A \text{ xor } B \text{ xor } C$


$F6 = A \text{ xor } B \text{ xor } C$

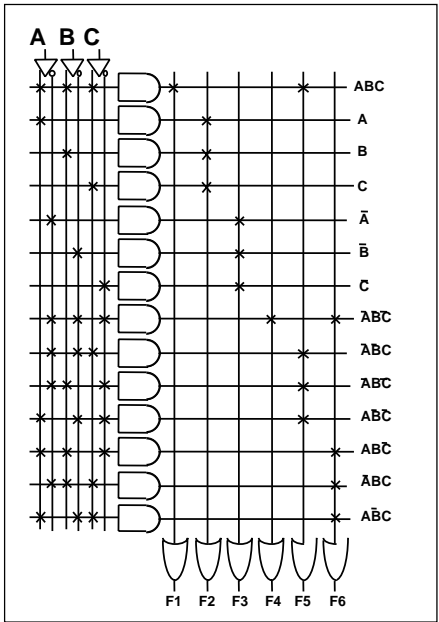

PALs and PLAs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 PAL concept : implemented by Monolithic Memories
(substrate is active materialsuch as semiconductor silicon)
programmable AND array but constrained topology of the OR Array
connections between product terms are hardwired
the higher the OR gate fanins, the fewer the functional outputs from PAL



A given column of the OR array has access to only a subset of the possible product terms

PLA concept : generalized topologies in AND and OR planes
take advantage of shared product terms
slower

4-9


PALs and PLAs

Design Example: BCD to Gray Code Converter

Truth Table

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

K-maps

 

Minimized Functions:

$$W = A + B D + B C$$

$$X = B C'$$


$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

4-10

PALs and PLAs

Programmed PAL:

 


4 product terms per each OR gate

4-11

PALs and PLAs

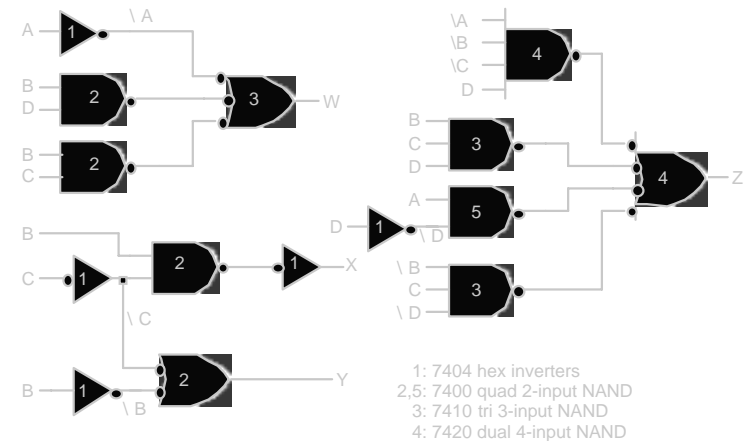Code Converter Discrete Gate Implementation





4 SSI Packages vs. 1 PLA/PAL Package!

4-12

PALs and PLAs

Another Example: Magnitude Comparator

$AB=CD$ $AB \neq CD$ $AB < CD$ $AB > CD$

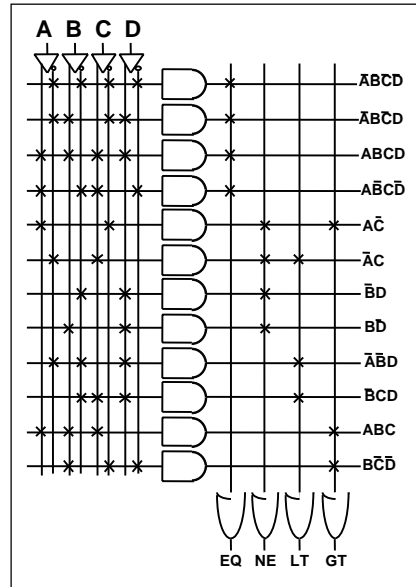 

4-13

Non-Gate Logic

Introduction

AND-OR-Invert
PAL/PLA

Generalized Building Blocks
Beyond Simple Gates


Kinds of "Non-gate logic":

- switching circuits built from CMOS transmission gates
- multiplexer/selecter functions
- decoders
- tri-state and open collector gates
- read-only memories

4-14

Steering Logic: Switches

Voltage Controlled Switches

 

"n-Channel MOS"

Metal Gate, Oxide, Silicon Sandwich

Diffusion regions: negatively charged ions driven into Si surface


Si Bulk: positively charged ions

By "pulling" electrons to the surface, a conducting channel is formed


4-15

Steering Logic

Voltage Controlled Switches

 

 Logic 1 on gate,
Source and Drain connected




Logic 0 on gate,
Source and Drain connected

4-16

Steering Logic

Logic Gates from Switches

 

Inverter

NAND Gate

NOR Gate


Pull-up network constructed from pMOS transistors

Pull-down network constructed from nMOS transistors

4-17

Steering Logic

Inverter Operation

 


Input is 1
Pull-up does not conduct
Pull-down conducts
Output connected to GND

Input is 0
Pull-up conducts
Pull-down does not conduct
Output connected to VDD

4-18

Steering Logic

NAND Gate Operation

 


A = 1, B = 1
Pull-up network does not conduct
Pull-down network conducts
Output node connected to GND

A = 0, B = 1
Pull-up network has path to VDD
Pull-down network path broken
Output node connected to VDD

4-19

Steering Logic

NOR Gate Operation

 

A = 0, B = 0
Pull-up network conducts
Pull-down network broken
Output node at VDD

A = 1, B = 0
Pull-up network broken
Pull-down network conducts
Output node at GND

4-20


Steering Logic

CMOS Transmission Gate

nMOS transistors good at passing 0's but bad at passing 1's
produce weak 1

pMOS transistors good at passing 1's but bad at passing 0's
produce weak 0

 perfect "transmission" gate places these in parallel:




4-21


Steering Logic

Selection Function/Demultiplexer Function with Transmission Gates

 Selector:
Choose I0 if S = 0
Choose I1 if S = 1



 
Demultiplexer:
I to Z0 if S = 0
I to Z1 if S = 1



4-22

Steering Logic

 Use of Multiplexer/Demultiplexer in Digital Systems



So far, we've only seen point-to-point connections among gates


Mux/Demux used to implement multiple source/multiple destination interconnect

4-23

Steering Logic

Well-formed Switching Networks

 Problem with the Demux implementation:
multiple outputs, but only one connected to the input!



The fix: additional logic to drive every output to a known value

Never allow outputs to "float"


4-24

Steering Logic


Complex Steering Logic Example

N Input Tally Circuit: count # of 1's in the inputs


I_1	Zero	One
0	1	0
1	0	1

 

 Conventional Logic for 1 Input Tally Function



 
Switch Logic Implementation of Tally Function




Steering Logic

Complex Steering Logic Example

Operation of the 1 Input Tally Circuit

 

 
Input is 0, straight through switches enabled




Steering Logic

Complex Steering Logic Example

Operation of 1 input Tally Circuit

 

Input = 1, diagonal switches enabled

 


Steering Logic

Complex Steering Logic Example

Extension to the 2-input case

I_1	I_2	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

 


Conventional logic implementation

Steering Logic

Complex Steering Logic Example

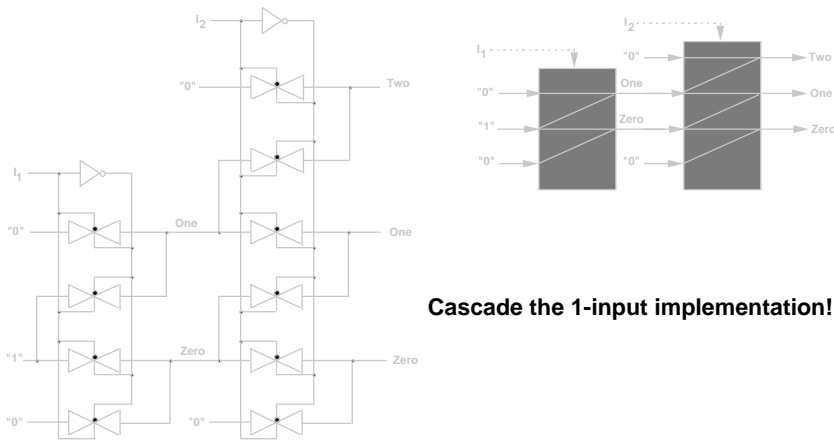
Switch Logic Implementation: 2-input Tally Circuit



Steering Logic

Complex Steering Logic Example


Operation of 2-input implementation

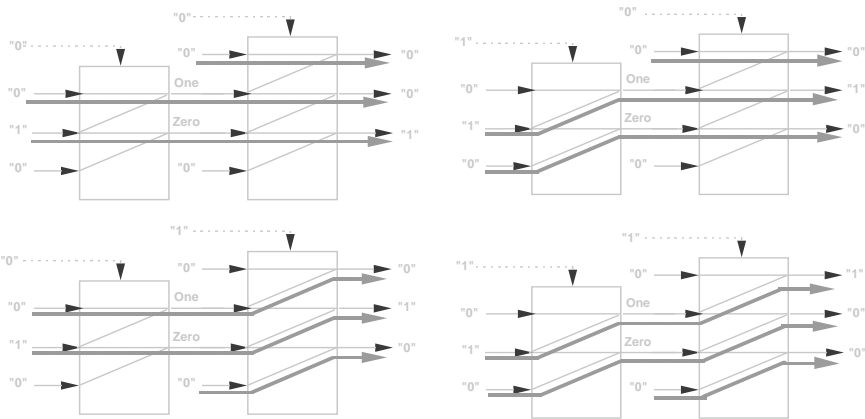

Multiplexers/Selectors

Use of Multiplexers/Selectors

Multi-point connections

 

Multiplexers/Selectors

General Concept

2^n data inputs, n control inputs, 1 output
used to connect 2^n points to a single point
control signal pattern form binary index of input connected to output

$$Z = A' I_0 + A I_1$$

Functional form


A	Z
0	I_0
1	I_1

Logical form


I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Two alternative forms
for a 2:1 Mux Truth Table


Multiplexers/Selectors

 

$$Z = A' I_0 + A I_1$$

 
 
$$Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$




$$Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$

In general, $Z = \sum_{k=0}^{2^n-1} m_k I_k$
in minterm shorthand form for a $2^n:1$ Mux

4-33


Multiplexers/Selectors

Alternative Implementations

 

Gate Level
Implementation
of 4:1 Mux

thirty six transistors

 


Transmission Gate
Implementation
of 4:1 Mux

twenty transistors

4-34

Multiplexer/Selector


Large multiplexers can be implemented by cascaded smaller ones

 

Alternative 8:1 Mux Implementation

Control signals B and C simultaneously
choose one of I0-I3 and I4-I7

 Control signal A chooses which of the
upper or lower MUX's output to gate to Z



4-35

Multiplexer/Selector

Multiplexers/selectors as a general purpose logic block

$2^{n-1}:1$ multiplexer can implement any function of n variables


n-1 control variables; remaining variable is a data input to the mux

Example:

$$F(A,B,C) = m_0 + m_2 + m_6 + m_7$$


$$= A' B' C' + A' B C' + A B C' + A B C$$
 
$$= A' B' (C') + A' B (C') + A B' (0) + A B (1)$$



"Lookup Table"


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

4-36


Multiplexer/Selector

Generalization

 

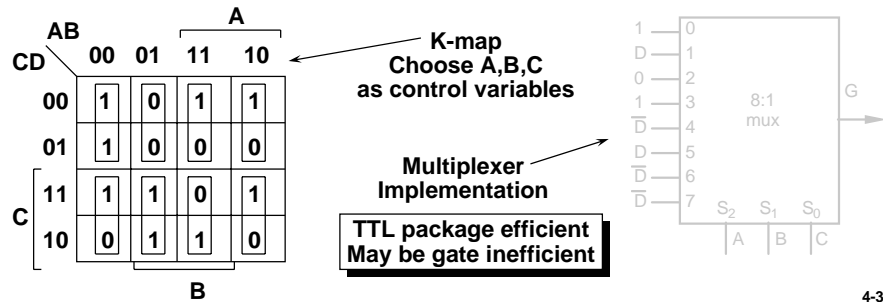Example:


G(A,B,C,D) can be implemented by an 8:1 MUX:



4-37

Multiplexer/Selector

- TTL quad 2:1 multiplexers with enable

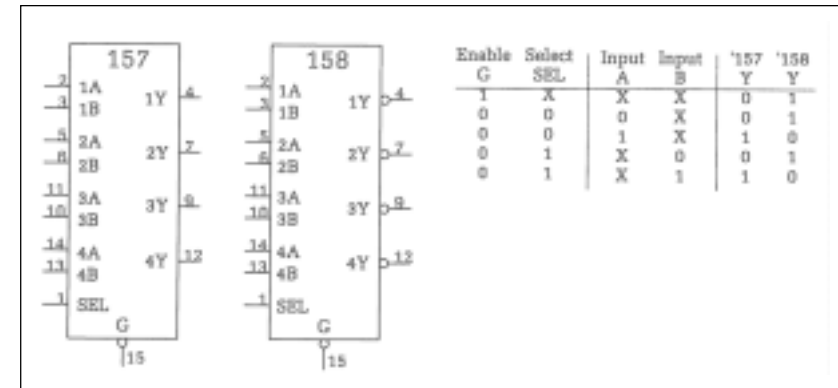

4-38

Decoders/Demultiplexers

Decoder: single data input, n control inputs, 2^n outputs

control inputs (called select S) represent Binary index of output to which the input is connected

data input usually called "enable" (G)

1:2 Decoder:

$$O0 = G \cdot \overline{S}; \quad O1 = G \cdot S$$

3:8 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1} \cdot \overline{S2}$$

$$O1 = G \cdot \overline{S0} \cdot \overline{S1} \cdot S2$$

$$O2 = G \cdot \overline{S0} \cdot S1 \cdot \overline{S2}$$

$$O3 = G \cdot \overline{S0} \cdot S1 \cdot S2$$

$$O4 = G \cdot S0 \cdot \overline{S1} \cdot \overline{S2}$$

$$O5 = G \cdot S0 \cdot \overline{S1} \cdot S2$$

$$O6 = G \cdot S0 \cdot S1 \cdot \overline{S2}$$

$$O7 = G \cdot S0 \cdot S1 \cdot S2$$

2:4 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1}$$


$$O1 = G \cdot \overline{S0} \cdot S1$$

$$O2 = G \cdot S0 \cdot \overline{S1}$$

$$O3 = G \cdot S0 \cdot S1$$


Decoders/Demultiplexers

Alternative Implementations

 

1:2 Decoder, Active High Enable

1:2 Decoder, Active Low Enable

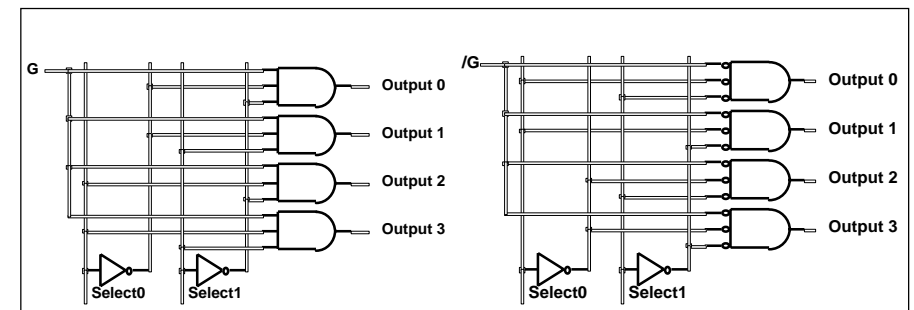

2:4 Decoder, Active High Enable


2:4 Decoder, Active Low Enable

4-39


4-40

Decoders/Demultiplexers

Switch Logic Implementations

 

Naive, Incorrect Implementation
All outputs not driven at all times

 


Correct 1:2 Decoder Implementation

4-41

Decoders/Demultiplexers

Switch Implementation of 2:4 Decoder

 

Operation of 2:4 Decoder

$S_0 = 0, S_1 = 0$


one straight thru path

three diagonal paths

4-42

Decoder/Demultiplexer

Decoder as a Logic Building Block

 

Decoder Generates Appropriate Minterm based on Control Signals

Example Function:

$$F_1 = A' B C' D + A' B' C D + A B C D$$


$$F_2 = A B C' D' + A B C$$

$$F_3 = (A' + B' + C' + D')$$

4-43

Decoder/Demultiplexer


Decoder as a Logic Building Block

 

If active low enable, then use NAND gates!

4-44


- **TTL decoder components**

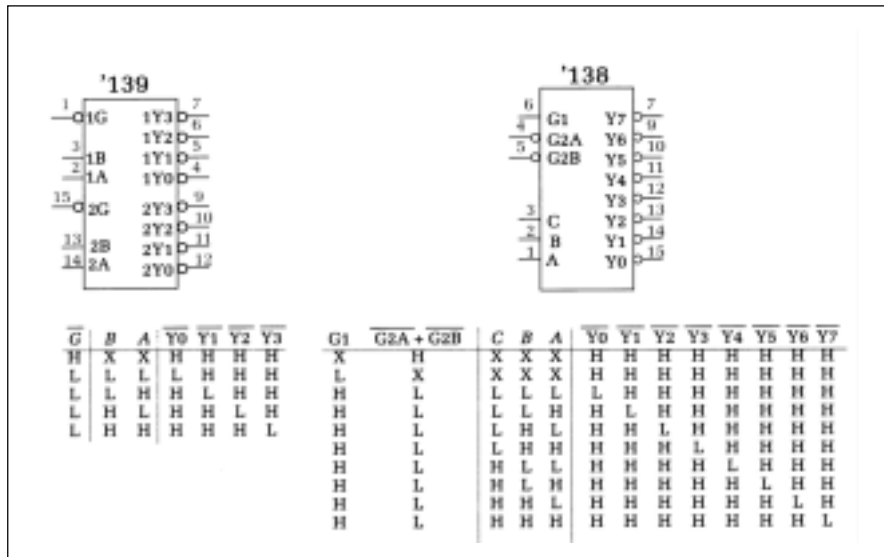

4-45

Multiplexers/Decoders

Alternative Implementations of 32:1 Mux

 


Multiplexer Only

Multiplexer + Decoder

Multiplexers/Decoders

5:32 Decoder

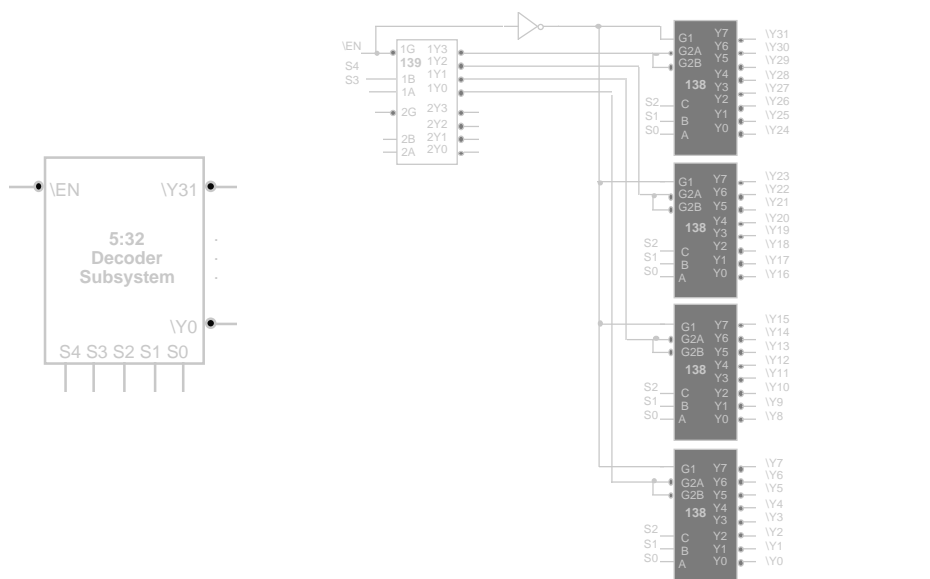

4-47

Tri-State and Open-Collector

The Third State

Logic States: "0", "1"

Don't Care/Don't Know State: "X" (must be some value in real circuit!)

Third State: "Z" — high impedance — infinite resistance, no connection


Tri-state gates: output values are "0", "1", and "Z"
additional input: output enable (OE)

When OE is high, this gate is a non-inverting "buffer"

When \overline{OE} is low, it is as though the gate was *disconnected* from the output!

This allows more than one gate to be connected to the same output wire, as long as only one has its output enabled *at the same time*


Non-inverting buffer's timing waveform

 

4-48

Tri-state and Open Collector

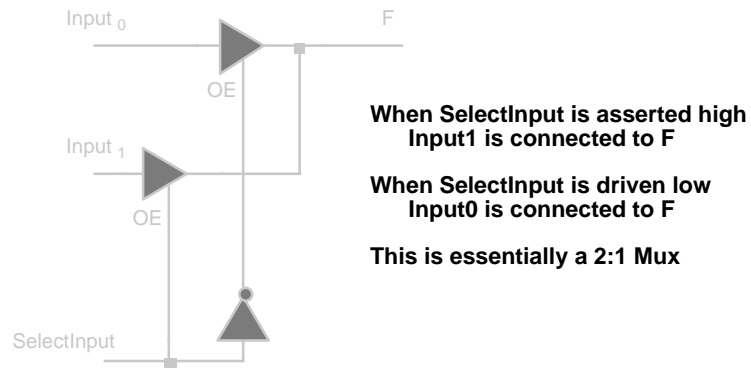
Using tri-state gates to implement an economical multiplexer:



4-49

Tri-state and Open Collector


Alternative Tri-state Fragment

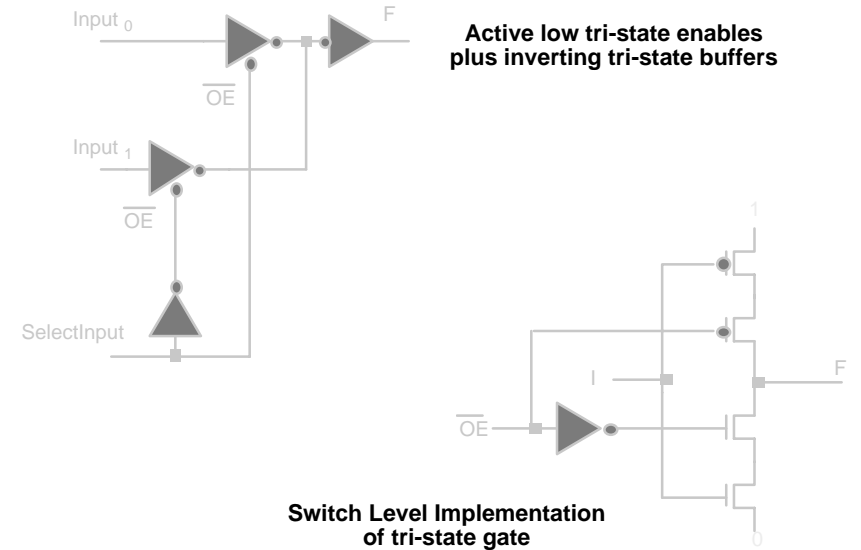

4-50

Tri-State and Open Collector

4:1 Multiplexer, Revisited

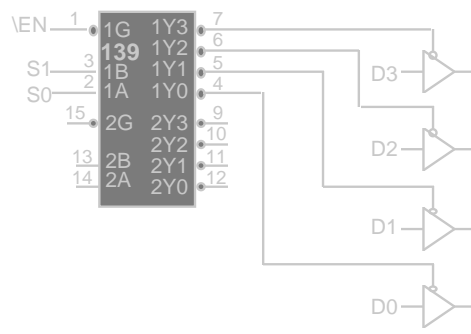

Decoder + 4 tri-state Gates

4-51


Tri-State and Open Collector

Open Collector

another way to connect multiple gates to the same output wire

gate only has the ability to pull its output low; it cannot actively drive the wire high


 
this is done by pulling the wire up to a logic 1 voltage through a resistor



OC NAND gates

Wired AND:

  
If A and B are "1", output is actively pulled low
if C and D are "1", output is actively pulled low
if one gate is low, the other high, then low wins
if both gates are "1", the output floats, pulled high by resistor
Hence, the two NAND functions are AND'd together!



4-52

Tri-State and Open Collector

4:1 Multiplexer

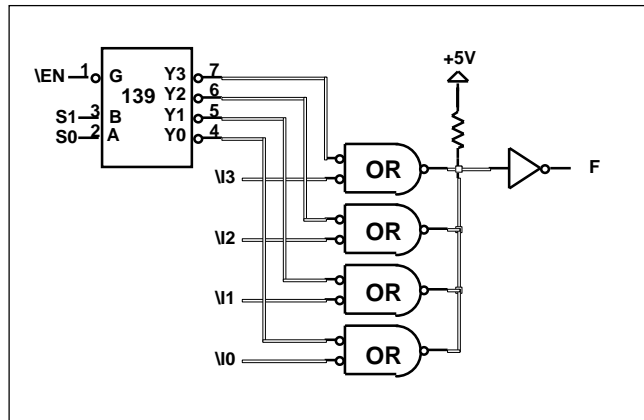


Decoder + 4 Open Collector Gates

4-53

Tri-State and Open Collector

- TTL tri-state buffers

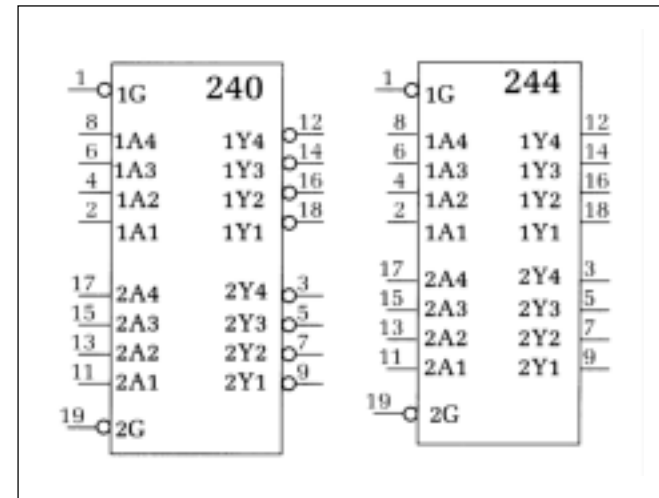

4-54


Read-Only Memories

ROM: Two dimensional array of 1's and 0's

Row is called a "word"; index is called an "address"

Width of row is called *bit-width* or *wordsize*

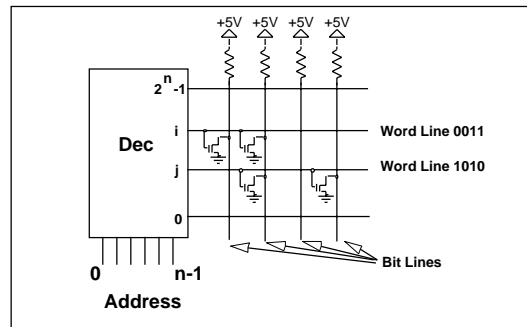Address is input, selected word is output



Internal Organization

4-55

Read-Only Memories


Example: Combination Logic Implementation

$$F_0 = A' B' C + A B' C' + A B' C$$

$$F_1 = A' B' C + A' B C' + A B C$$

$$F_2 = A' B' C' + A' B' C + A B' C'$$


$$F_3 = A' B C + A B' C' + A B C'$$

 

4-56

Read-Only Memories

 Not unlike a PLA structure with a fully decoded AND array!



ROM vs. PLA:

ROM approach advantageous when

- (1) design time is short (no need to minimize output functions)
- (2) most input combinations are needed (e.g., code converters)
- (3) little sharing of product terms among output functions

ROM problem: size doubles for each additional input, can't use don't cares

PLA approach advantageous when


- (1) design tool like espresso is available
- (2) there are relatively few unique minterm combinations
- (3) many minterms are shared among the output functions

PAL problem: constrained fan-ins on OR planes


4-57

Read-Only Memories

2764 EPROM
8K x 8

 

16K x 16
Subsystem

 

4-58

Combinational Logic Word Problems

General Design Procedure

1. Understand the Problem
 - what is the circuit supposed to do?
 - write down inputs (data, control) and outputs
 - draw block diagram or other picture
2. Formulate the Problem in terms of a truth table or other suitable design representation
 - truth table or waveform diagram
3. Choose Implementation Target
 - ROM, PAL, PLA, Mux, Decoder + OR, Discrete Gates
4. Follow Implementation Procedure
 - K-maps, espresso, misII

4-59

Combinational Logic Word Problems

Process Line Control Problem

Statement of the Problem

Rods of varying length (+/-10%) travel on conveyor belt
Mechanical arm pushes rods within spec (+/-5%) to one side
Second arm pushes rods too long to other side
Rods too short stay on belt

3 light barriers (light source + photocell) as sensors

Design combinational logic to activate the arms

Understanding the Problem

Inputs are three sensors, outputs are two arm control signals

Assume sensor reads "1" when tripped, "0" otherwise


Call sensors A, B, C

Draw a picture!

4-60

Combinational Logic Word Problems

Process Control Problem

 


Where to place the light sensors A, B, and C to distinguish among the three cases?

Assume that A detects the leading edge of the rod on the conveyor

4-61

Combinational Logic Word Problems

Process Control Problem

 

A to B distance place apart at specification - 5%

A to C distance placed apart at specification +5%

4-62

Combinational Logic Word Problems

Process Control Problem

A	B	C	Function
0	0	0	X
0	0	1	X
0	1	0	X
0	1	1	X
1	0	0	too short
1	0	1	X
1	1	0	in spec
1	1	1	too long

Truth table and logic implementation now straightforward

"too long" = $A B C$
(all three sensors tripped)

"in spec" = $A B C'$
(first two sensors tripped)

4-63

Combinational Logic Word Problems

BCD to 7 Segment Display Controller



Understanding the problem:

input is a 4 bit bcd digit

output is the control signals for the display

4 inputs A, B, C, D

7 outputs C0 ~ C6

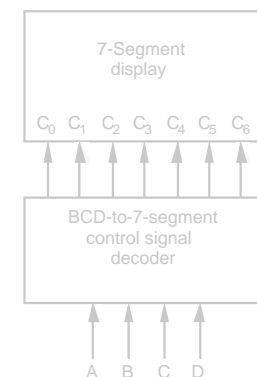 

Block Diagram

4-64

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

Formulate the problem in terms of a truth table

Choose implementation target:

if ROM, we are done

don't cares imply PAL/PLA may be attractive

Follow implementation procedure:

hand reduced K-maps


vs.

espresso

4-65

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

 

$$\begin{aligned} C0 &= A + B D + C + B' D' \\ C1 &= A + C' D' + C D + B' \\ C2 &= A + B + C' + D \end{aligned}$$

14 Unique Product Terms


$$\begin{aligned} C3 &= B' D' + C D' + B C' D + B' C \\ C4 &= B' D' + C D \\ C5 &= A + C' D' + B D' + B C' \\ C6 &= A + C D' + B C' + B' C \end{aligned}$$

4-66

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

16H8PAL
Can Implement
the function

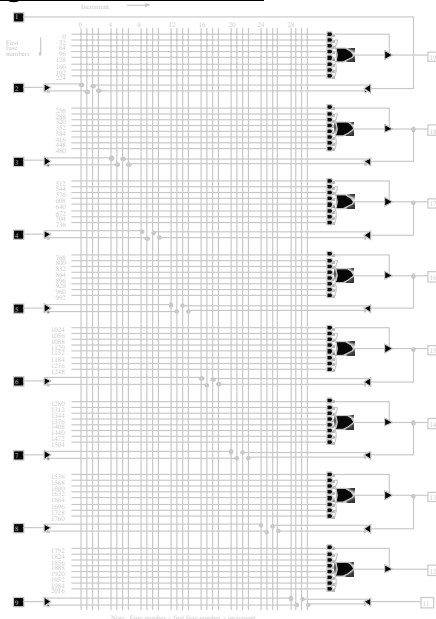


4-67

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

14H8PAL
Cannot Implement
the function

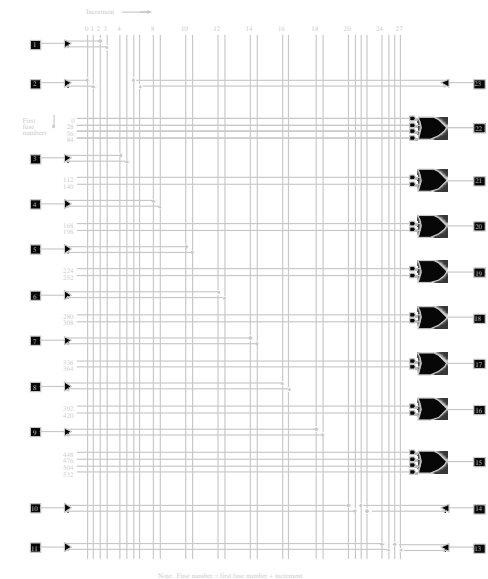


4-68

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

F100 PAL programming map

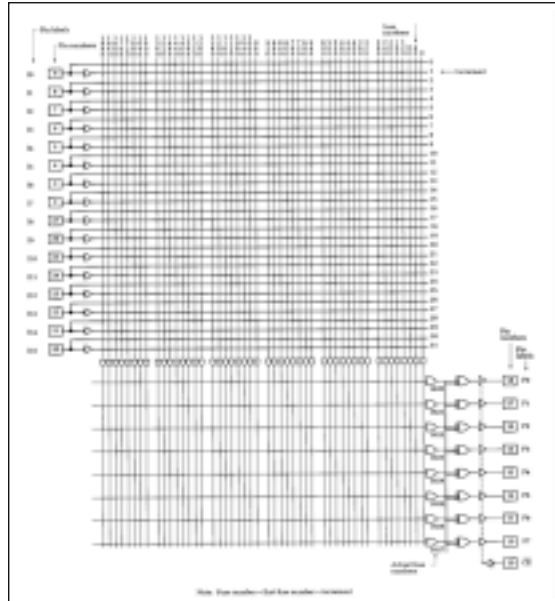

4-69

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

```
.i 4
.o 7
.ilb a b c d
.ob c0 c1 c2 c3 c4 c5 c6
.p 16
0000 1111110
0001 0110000
0010 1101101
0011 1111001
0100 0110011
0101 1011011
0110 1011111
0111 1110000
1000 1111111
1001 1110011
1010 -----
1011 -----
1100 -----
1101 -----
1110 -----
1111 -----
.e
```

espresso
input

```
.i 4
.o 7
.ilb a b c d
.ob c0 c1 c2 c3 c4 c5 c6
.p 9
-10- 0000001
-01- 0001001
-0-1 0110000
-101 1011010
--00 0110010
--11 1110000
-0-0 1101100
1--- 1000011
-110 1011111
.e
```

espresso
output

$C0 = B' C' D + C D + B' D' + B C D' + A$
 $C1 = B' D + C' D' + C D + B' D'$
 $C2 = B' D + B C' D + C' D' + C D + B C D'$
 $C3 = B C' D + B' D + B' D' + B C D'$
 $C4 = B' D' + B C D'$
 $C5 = B C' D + C' D' + A + B C D'$
 $C6 = B' C + B C' + B C D' + A$

9 Unique Product Terms!


63 Literals, 20 Gates

4-70

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

PLA Implementation

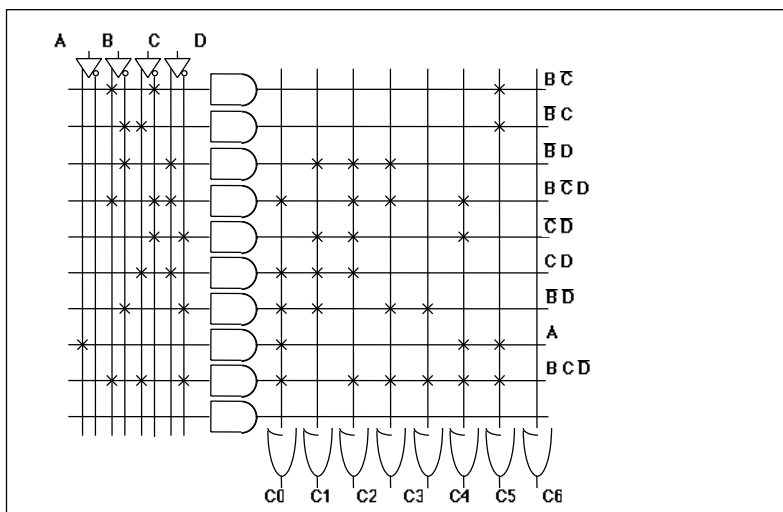

4-71

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

Multilevel Implementation

$$X = C' + D'$$

$$Y = B' C'$$

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

52 literals

33 gates

Ineffective use of don't cares

4-72

Combinational Logic Word Problems

Logical Function Unit

Statement of the Problem:

3 control inputs: C0, C1, C2
2 data inputs: A, B
1 output: F

C0	C1	C2	F	Comments
0	0	0	1	always 1
0	0	1	A + B	logical or
0	1	0	$\overline{A \cdot B}$	logical nand
0	1	1	A xor B	logical xor
1	0	0	A xnor B	logical xnor
1	0	1	A · B	logical and
1	1	0	$\overline{A + B}$	logical nor
1	1	1	0	always 0

4-73

Combinational Logic Word Problems

Logical Function Unit


Formulate as a truth table

Choose implementation technology

5-variable K-map

espresso

multiplexor implementation

 


4-74

Combinational Logic Word Problems

Logical Function Unit

Follow implementation procedure

 

$$F = C2' A' B' + C0' A B' + C0' A' B + C1' A B$$

5 gates, 5 inverters

Also four packages:
4 x 3-input NAND
1 x 4-input NAND

Alternative: 32 x 1-bit ROM

single package

4-75

Combinational Logic Word Problems

8-Input Barrel Shifter

Specification:

Inputs: D7, D6, ~ D0
Outputs: O7, O6, ~ O0
Control: S2, S1, S0

shift input the specified number
of positions to the right

Understand the problem:

D7 → O7
D6 → O6
D5 → O5
D4 → O4
D3 → O3
D2 → O2
D1 → O1
D0 → O0
S2, S1, S0 = 0 0 0

D7 → O7
D6 → O6
D5 → O5
D4 → O4
D3 → O3
D2 → O2
D1 → O1
D0 → O0
S2, S1, S0 = 0 0 1

D7 → O7
D6 → O6
D5 → O5
D4 → O4
D3 → O3
D2 → O2
D1 → O1
D0 → O0
S2, S1, S0 = 0 1 0

4-76

Combinational Logic Word Problems

8-Input Barrel Shifter

Function Table

S2	S1	S0	O7	O6	O5	O4	O3	O2	O1	O0
0	0	0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	1	D6	D5	D4	D3	D2	D1	D0	D7
0	1	0	D5	D4	D3	D2	D1	D0	D7	D6
0	1	1	D4	D3	D2	D1	D0	D7	D6	D5
1	0	0	D3	D2	D1	D0	D7	D6	D5	D4
1	0	1	D2	D1	D0	D7	D6	D5	D4	D3
1	1	0	D1	D0	D7	D6	D5	D4	D3	D2
1	1	1	D0	D7	D6	D5	D4	D3	D2	D1

Boolean equations

$$O7 = S2' S1' S0' D7 + S2' S1' S0 D6 + \dots + S2 S1 S0 D0$$

$$O6 = S2' S1' S0' D6 + S2' S1' S0 D5 + \dots + S2 S1 S0 D7$$

$$O5 = S2' S1' S0' D5 + S2' S1' S0 D4 + \dots + S2 S1 S0 D6$$

$$O4 = S2' S1' S0' D4 + S2' S1' S0 D3 + \dots + S2 S1 S0 D5$$

$$O3 = S2' S1' S0' D3 + S2' S1' S0 D2 + \dots + S2 S1 S0 D4$$

$$O2 = S2' S1' S0' D2 + S2' S1' S0 D1 + \dots + S2 S1 S0 D3$$

$$O1 = S2' S1' S0' D1 + S2' S1' S0 D0 + \dots + S2 S1 S0 D2$$

$$O0 = S2' S1' S0' D0 + S2' S1' S0 D7 + \dots + S2 S1 S0 D1$$

4-77


Combinational Logic Word Problems

8-Input Barrel Shifter


Straightforward gate logic implementation OR

8 by 8:1 multiplexer (wiring mess!) OR

Switch logic

 

Crosspoint switches

 

Fully Wired crosspoint switch

4-78

Chapter Review

• Non-Simple Gate Logic Building Blocks:

PALs/PLAs

Multiplexers/Selectors

Decoders

ROMs

Tri-state, Open Collector

• Combinational Word Problems:

Understand the Problem

Formulate in terms of a Truth Table

Choose implementation technology

Implement by following the design procedure

4-79